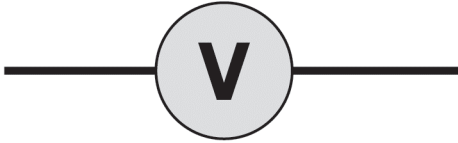


**Goal** • Learn to understand and draw circuit symbols.



**conducting wire**



**voltmeter**



**battery**



**open switch**



# Circuit Symbols



**closed switch**



**load**



**ammeter**

