

Chapter 5 Practice Test

For questions 1 to 6, write the term from column B that completes the statement in column A.

A	B
1. Voltage is measured in _____.	a) current
2. Electric current is measured in _____.	b) amperes (A)
3. An electric _____ is a pathway for the flow of an electric _____.	c) potential difference
4. A _____ provides more than one complete pathway for electric current.	d) volts (V)
5. Another term for voltage is _____.	e) circuit
6. A _____ provides only one complete pathway for electric current.	f) parallel circuit
	g) series circuit
	h) energy

7. Decide whether each of the following statements is true or false. If it is false, rewrite it to make it true.

a) True/False An electric current is larger when it enters a load.

b) True/False If an electric circuit has two loads, the voltage across each load will be the same as the voltage across the source.

c) True/False Energy is the ability to do work, such as making something move.

Name: _____

Date: _____

BLM 5-8
(continued)

8. List two uses for LEDs.

a) _____

b) _____

9. a) Add the symbols for a battery, bulb, and switch to the circuit diagram shown.



b) On the diagram, show where you would connect a voltmeter to measure the voltage across the load.



10. a) Complete the flowchart to show how a light bulb converts electric energy to another form of useful energy.

_____ → _____ → _____

b) Complete the flowchart to show how a light bulb converts electric energy to waste energy.

_____ → _____ → _____

11. a) Vanessa's CD player uses 3000 J in 60 s. What is the power rating of her CD player? Show your work.

$$\text{Power (W)} = \frac{\text{Energy (J)}}{\text{Time (s)}}$$

b) Vanessa uses her CD player for 30 h. How much energy in kWh does the CD player use during this time? Show your work.

$$\text{Energy} = \text{Power} \times \text{Time} \quad 1 \text{ kW} = 1000 \text{ W}$$

c) If 1 kWh costs 9.0¢, how much did it cost for Vanessa to use her CD player? Show your work.