

Name: _____

Date: _____

BLM 7-5


Label the Circuit Diagrams

Choose the correct term from the box to label each circuit diagram.


series circuit

parallel circuit


combination circuit

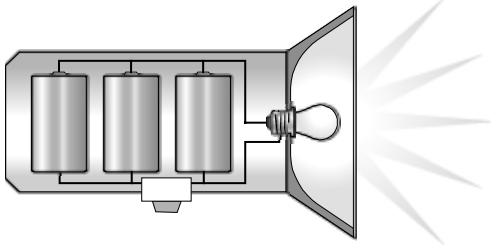


1. _____

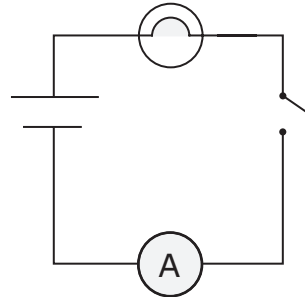


4. _____

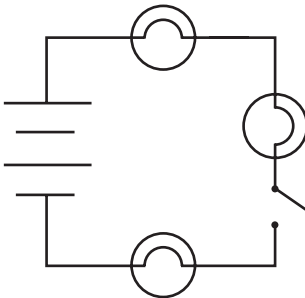


2. _____

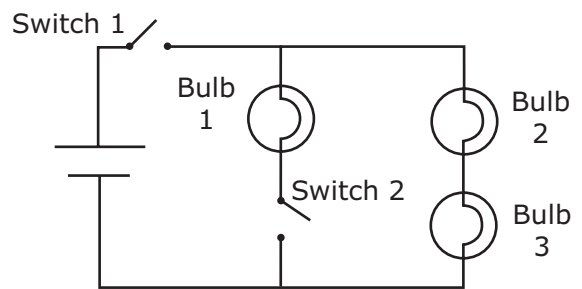

5. _____

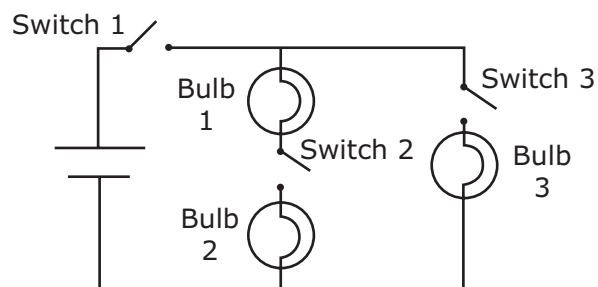

3. _____

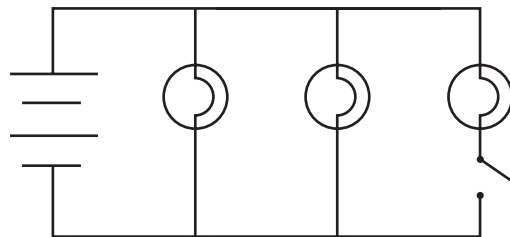

6. _____