
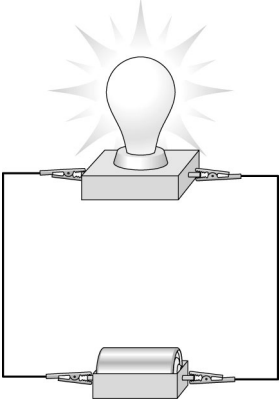


Circuit Diagrams

1. Use the correct symbols to draw each of these circuits.

2. Examine this circuit illustration.

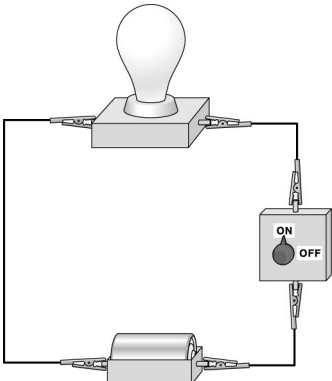- a) How many batteries does this circuit contain? _____
- b) Draw a box around any batteries in this circuit.
- c) How many bulbs does this circuit contain? _____
- d) Put an X on any bulbs in this circuit.
- e) How many switches does this circuit contain? _____
- f) Circle any switches in this circuit.

