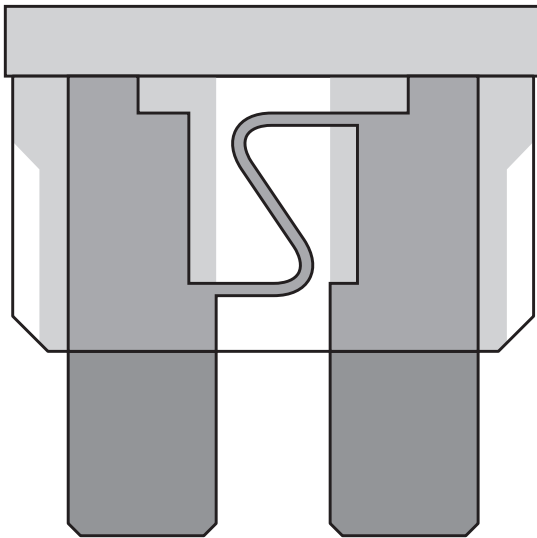


Name: _____


Date: _____

BLM 8-2


Fuses



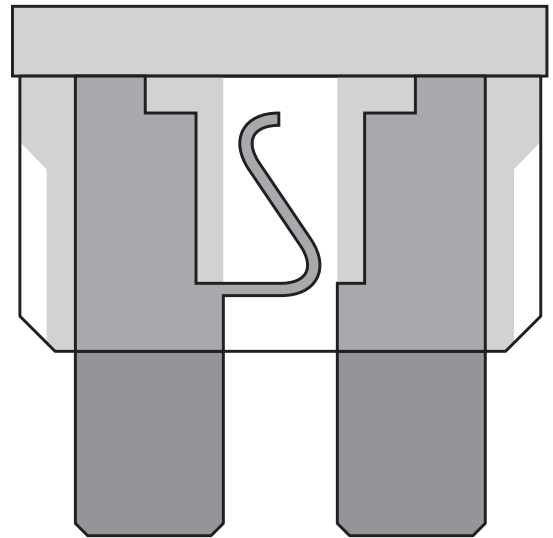A An intact fuse.
Current flows through
the wire inside the fuse.
The circuit is closed.



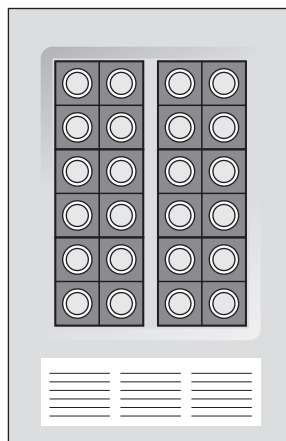B A "blown" fuse. The wire
has melted. Current does
not flow through the wire.
The circuit is open.



A fuse box. Many
buildings have
fuse boxes. Most
cars and trucks
also have fuse
boxes.