

Name: _____

Date: _____

BLM 8-3

Safe or Overloaded?

1. Under each circuit, write "safe" if the circuit is safe. Write "overloaded" if the circuit is overloaded. Show how you know.

