

CHAPTER 1**HANDOUT****In Series****BLM 1-7**

Goal • Use the table below to draw each circuit and to record your observations for Conduct an Investigation 1-H: In Series.

Diagram	Observations
Part 1: Sources in Series	
Step 1	
Steps 2 & 3	
Part 2: Loads in Series	
Step 4	
Steps 5 & 6	
Step 7	
Part 3: Circuit with a Switch	
Steps 8–11	