

Goal • Use the table below to draw each circuit and to record your observations for Conduct an Investigation 1-J: On Parallel Tracks.

Diagram	Observations
Step 1	
Step 2 & 3	
Step 4 & 5	